

Shri Shivaji Maratha Society's

Samaj Bhushan Baburao Alias Appasaheb Jedhe Art's Commerce & Science College, Pune - 02

B.Sc. (Computer Science) Internal Examination, Feb 2017

Electronics 2- Principles of Digital Electronics

Class: F.Y.B.Sc

Marks: 20

Q.1 Attempt the following:

[2×4=08]

- a) What is Multiplexer & Demultiplexer.
- b) What is two types of logic families.
- c) What is Encoder & Decoder.
- d) What is shift register & types of shift registers.

Q.2 Attempt Any three of the following:

[3×4=12]

- a) Explain J-K Flip/Flop with its logic diagram & truth table
- b) Write the parameters of Logic Families.
- c) Draw logic diagram & working of 4:1 Multiplexer in details.
- d) Explain the working Octal to Binary encoder.

Best of Luck
